

Student ID:	21201686	Lab Section:	13
Name:	Khandaker Rabiul Nasir	Lab Group:	01

### Experiment No. 1

## Introduction to Series and Parallel Circuit Connections

### Objective

The aim of this experiment is to acquaint students with series and parallel circuit connections and to properly identify them on a breadboard or from a schematic diagram.

### Theory

An electrical circuit is a continuous path through which electrical current flows. Amongst various circuit combinations, two prominent ones are called "Series" and "Parallel". For a connection to be called "Series", it must fulfil the following criteria:

- All the components must be connected *one after the other*.
- The *same current* must flow through all the components.

For instance, in the following circuit, we have  $N$  resistors:  $R_1, R_2, R_3, \dots, R_N$  connected one after another and the same current  $I$  is flowing through them. All of these series resistors can be combined into just one equivalent resistance,

$$R_{eq} = R_1 + R_2 + R_3 \dots + R_N = \sum_{i=1}^N R_i$$

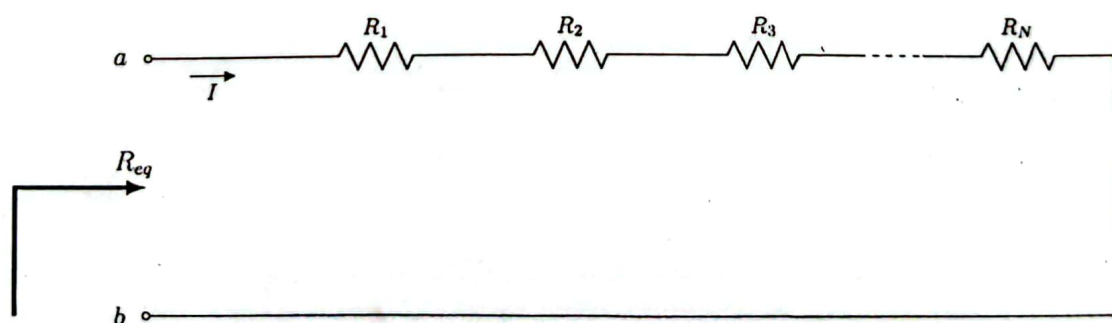


Figure: A series connection

Similarly, in a "Parallel" connection,

- All the components must be connected between the *same two nodes*.
- The *same potential (voltage) drop* should exist across all the components.

For example, in the following figure, we have  $N$  resistors with resistances:  $R_1, R_2, R_3, \dots, R_N$  connected at the same two nodes  $a$  and  $b$ . And therefore, the voltage drop across all the resistors are,  $\Delta V = V_a - V_b$ . Hence, we conclude that the resistors are connected in parallel. The equivalent resistance of these resistors is  $R_{eq}$  where,

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots + \frac{1}{R_N} = \sum_{i=1}^N \frac{1}{R_i}$$

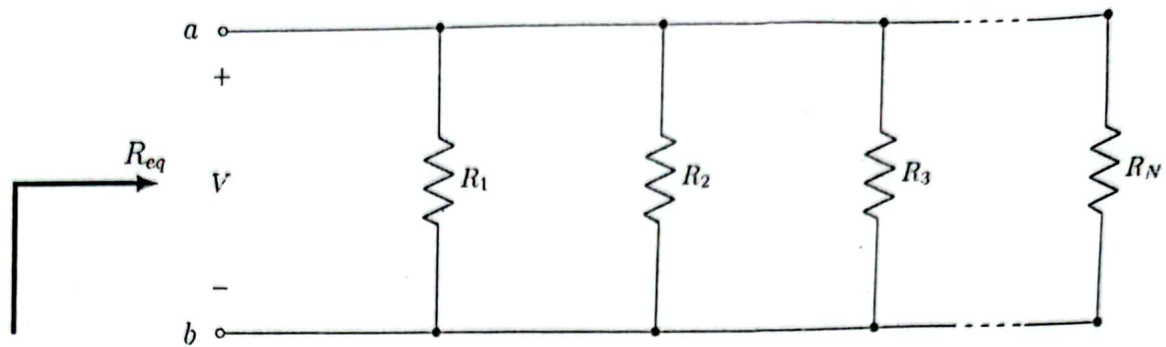


Figure: A parallel connection


In this experiment, we will learn how to connect circuits in breadboards and how to identify series and parallel connections,

## Apparatus


- Multimeter
- Resistors
- DC power supply
- Breadboard
- Jumper wires

## Procedures


- Measure the resistances of the provided resistors and fill up the data table.
- Construct the following circuits on a breadboard. Try to use minimum number of jumper wires:

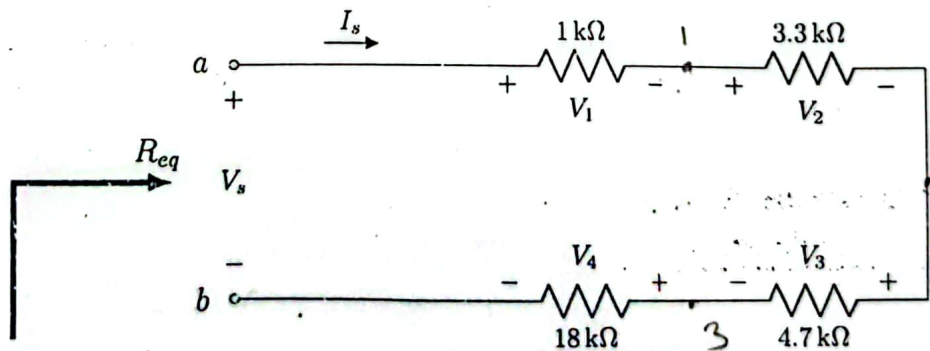

Circuit 1

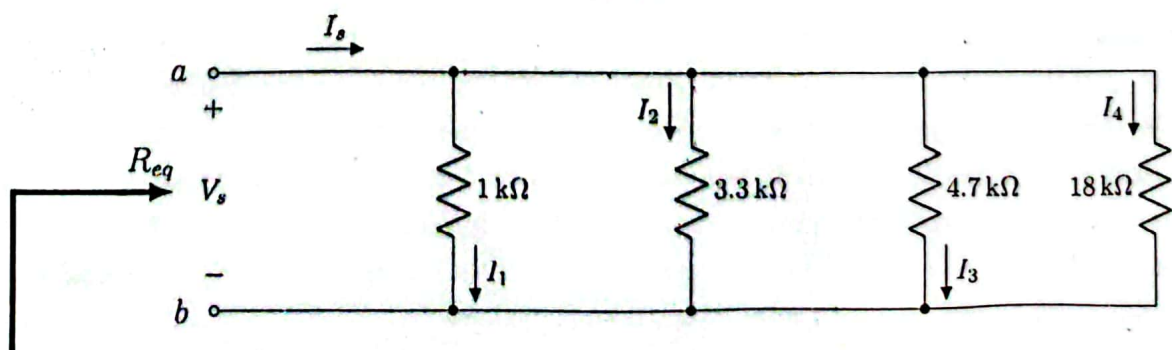

Circuit 2

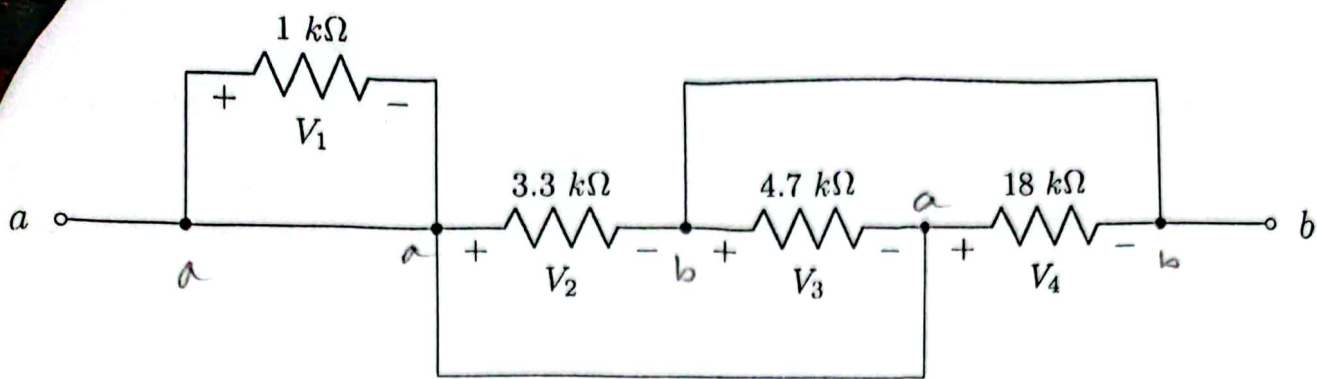

**Circuit 3**

- Measure the equivalent resistance using a multimeter. To do this, disconnect the power supply (if any) and connect the multimeter across the open terminals.
- Apply 6 V potential drop across the terminals *a* and *b*. Use the DC power supply to connect the positive terminal to node *a* and the negative terminal to terminal *b*.
- Measure the voltage and current across each resistor. Use Multimeter for measuring the voltage and use Ohm's law to calculate the current through each resistor. Fill up the data tables.

### Data Tables

Signature of Lab Faculty:

*[Handwritten Signature]*

Date:

*05-10-20*

*09-26-22*

\* For all the data tables, take data up to three decimal places, round to two, then enter into the table.

### Table 1: Resistance Data

For all your future calculations, please use the observed values only (even for theoretical calculations).

Notation	Expected Resistance	Observed Resistance (kΩ)
$R_1$	1 kΩ	1.00 kΩ
$R_2$	3.3 kΩ	3.275 kΩ
$R_3$	4.7 kΩ	4.61
$R_4$	18 kΩ	17.81



**Table 2: Data from Circuit 1**

In the following table,  $V_1$  is the voltage drop across resistor  $R_1$  and  $I_1$  is the current through it. Similar syntax applies to remaining resistors. For theoretical calculations, please note that, in series connection, the supplied voltage will be divided proportionally to the resistances. The voltage supplied to the complete circuit is denoted by  $V_s$  and the current being supplied to the whole network is denoted as  $I_s$ . Also, calculate the percentage of error between experimental and theoretical values of  $R_{eq}$ .

Observation	$R_{eq}$ (k $\Omega$ )	$V_s$ (V) (from dc power supply)	$V_s$ (V) (using multimeter)	$I_s = \frac{V_s}{R_{eq}}$ (mA)	$V_1$ (V)	$I_1 = \frac{V_1}{R_1}$ (mA)	$V_2$ (V)	$I_2 = \frac{V_2}{R_2}$ (mA)	$V_3$ (V)	$I_3 = \frac{V_3}{R_3}$ (mA)	$V_4$ (V)	$I_4 = \frac{V_4}{R_4}$ (mA)
Experimental	26.66	6.0	6.02	0.225	0.2209	0.2209	0.732	0.2235	1.037	0.222	4.02	0.225
Theoretical	26.29		6	0.228	0.222	0.227	0.738	0.227	1.0442	0.227	3.99	0.227

$$\text{Percentage of error} = \left| \frac{\text{Experimental} - \text{Theoretical}}{\text{Theoretical}} \right| \times 100\%$$

Here, Percentage of error in  $R_{eq}$  calculation = 1.407 %

**Table 3: Data from Circuit 2**

In a parallel connection, all the voltage drops are same across the components. Hence, we only need the supply voltage  $V_s$ . However, the current across each component is inversely proportional to the resistance values.

Observation	$R_{eq}$ (k $\Omega$ )	$V_s$ (V) (from dc power supply)	$V_s$ (V) (using multimeter)	$I_s = \frac{V_s}{R_{eq}}$ (mA)	$I_1 = \frac{V_s}{R_1}$ (mA)	$I_2 = \frac{V_s}{R_2}$ (mA)	$I_3 = \frac{V_s}{R_3}$ (mA)	$I_4 = \frac{V_s}{R_4}$ (mA)
Experimental	0.635	6.0	5.98	9.417	5.98	1.826	1.297	0.336
Theoretical	0.619		6	9.693	6	1.81	1.27	0.33

Here, Percentage of error in  $R_{eq}$  calculation = 9.69 %

Table 4: Data from Circuit 3

Collect the following data.

Experiment	$R_{ab}$ (k $\Omega$ )	$V_s$ (V) (from dc power supply)	$V_s$ (V) (using multimeter)	$I_s = \frac{V_s}{R_{eq}}$ (mA)	$V_1$ (V)	$I_1 = \frac{V_1}{R_1}$ (mA)	$V_2$ (V)	$I_2 = \frac{V_2}{R_2}$ (mA)	$V_3$ (V)	$I_3 = \frac{V_3}{R_3}$ (mA)	$V_4$ (V)	$I_4 = \frac{V_4}{R_4}$ (mA)
Experimental	1.73	6	6.02	3.48	0.0035	0.0035	6.01	1.835	-6.01	-1.302	6.01	0.337
Theoretical	1.75	6	6	3.49	0	0	6	1.81	6	1.27	6	0.33

Here, Percentage of error in  $R_{eq}$  calculation =


1.08 %

How are the resistors in circuit 3 connected with each other? Justify your answer.

The first resistor in the circuit is sorted and rest are connected with each other in a Parallel combination

## Questions

1.

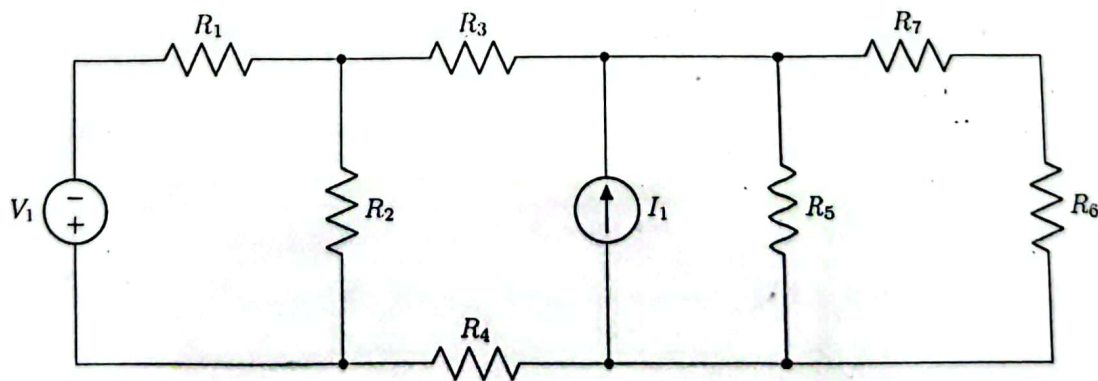

- (a) After taking voltage and currents measurements in a laboratory for the circuit shown above, the currents through the  $R_4$  and  $R_7$  resistors are found to be equal. Are  $R_4$  and  $R_7$  in series?

☐ Yes

☒ No



Justify your choice.

Using mesh analysis  $\epsilon I_1 \rightarrow \pi_1, i_2 = \frac{-I_2 P_3 + I_2 \pi_2}{V_3 + \pi_3 - \pi_2}$   
 And  $\epsilon I_1 \rightarrow \pi_3$  is  $i_4 = \frac{I_1 P_3}{P_2 + P_3}$   
 Hence, we see that  $i_2$  and  $i_4$  are different although they might be equal but that doesn't mean they are in series combination


(b)  $R_1, R_2$ , and  $R_3$  are connected in

☐ Series ☐ Parallel ☒ None of the two ☐ Cannot be predicted

Explain your choice.

$\pi_1, \pi_2$  and  $\pi_3$  are in mixture of both Parallel and series combination

2.

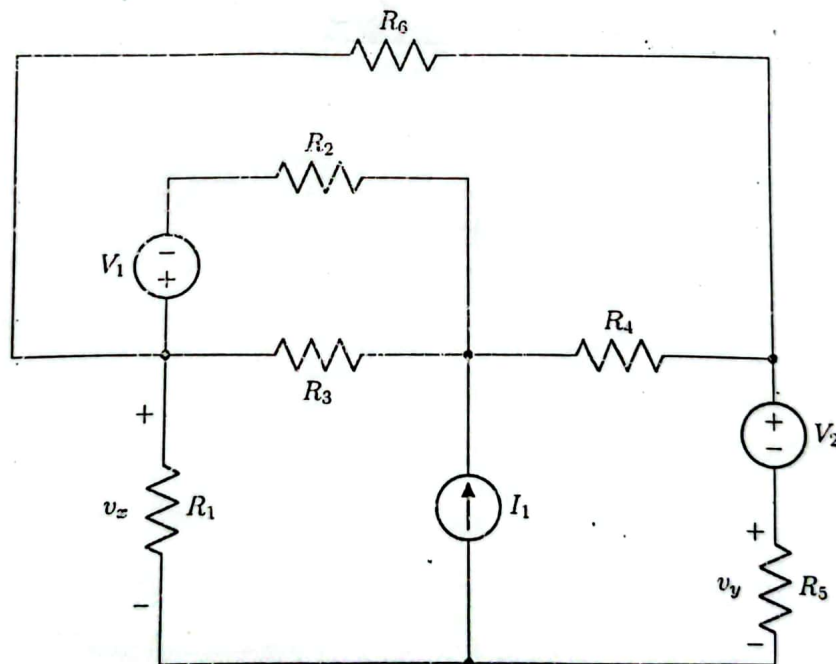


(a) If the voltages  $v_x$  and  $v_y$  are equal, are  $R_1$  and  $R_5$  in parallel?

☐ Yes ☒ No

Justify your answer.

No,  $R_1$  and  $R_5$  are not between some pair of nodes so they are not parallel

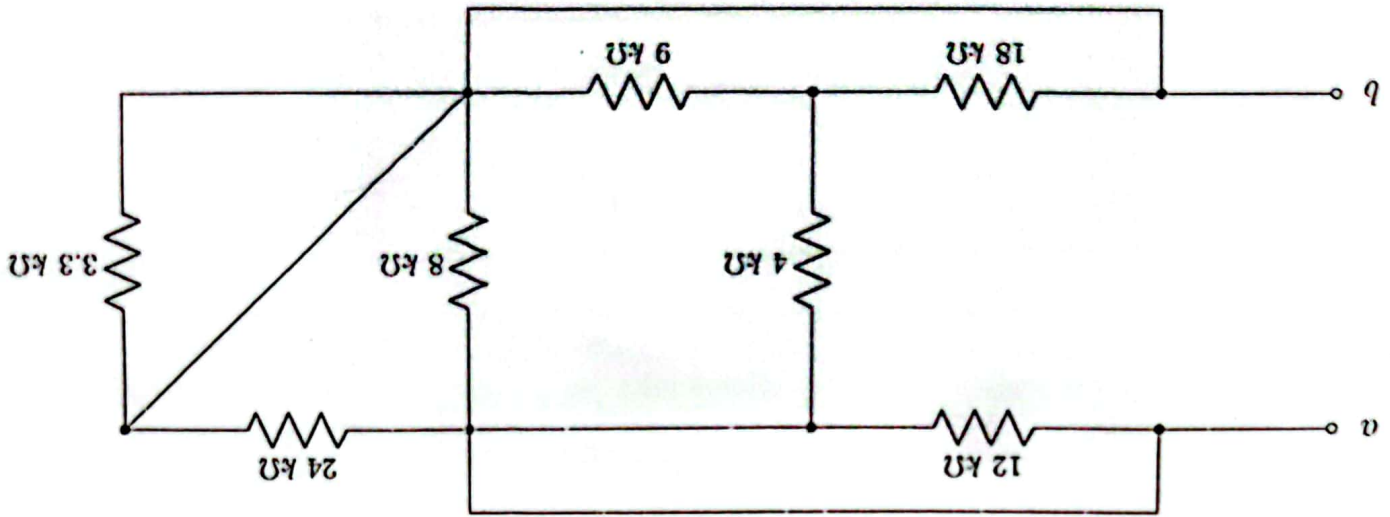
(a) How many nodes are there. Mark and label all the nodes in the circuit diagram.



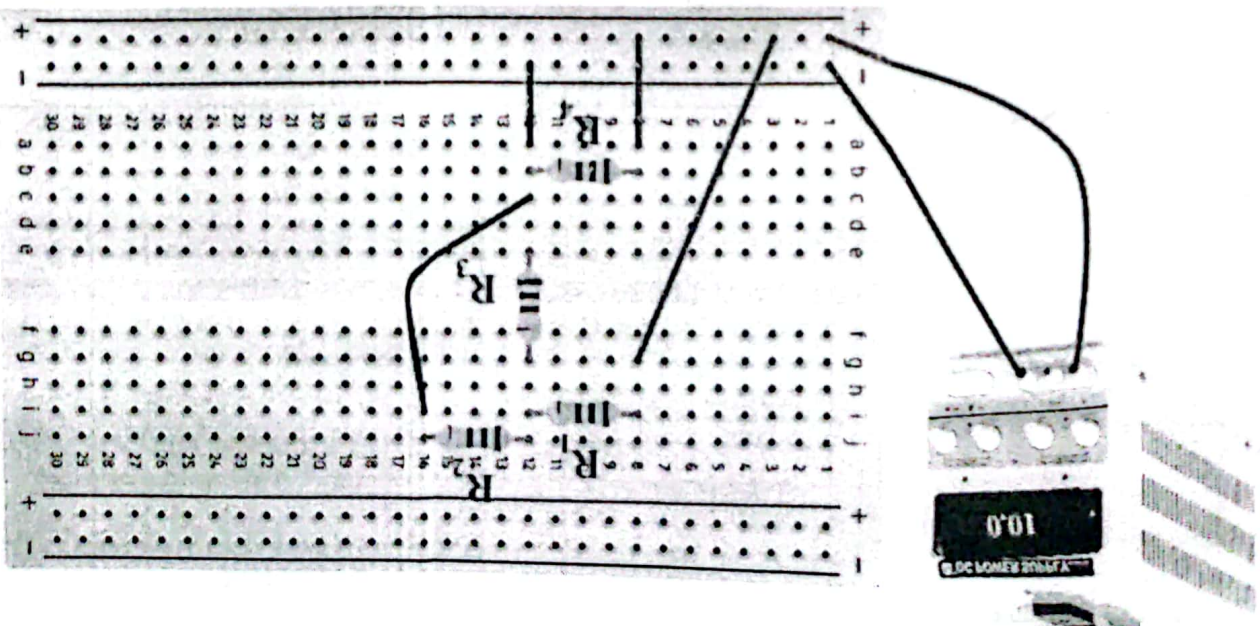4. For the following circuit:




Draw a circuit diagram of the circuit shown on the breadboard above.



ending nodes in each row that connect the corresponding circuit element.

Circuit Element	Starting/Ending Node	Ending/Starting Node
12 k $\Omega$ Resistor	a	c
4 k $\Omega$ Resistor	c	d
18 k $\Omega$ Resistor	b	d
9 k $\Omega$ Resistor	d	b
8 k $\Omega$ Resistor	b	a
24 k $\Omega$ Resistor	a	b
3.3 k $\Omega$ Resistor	b	b

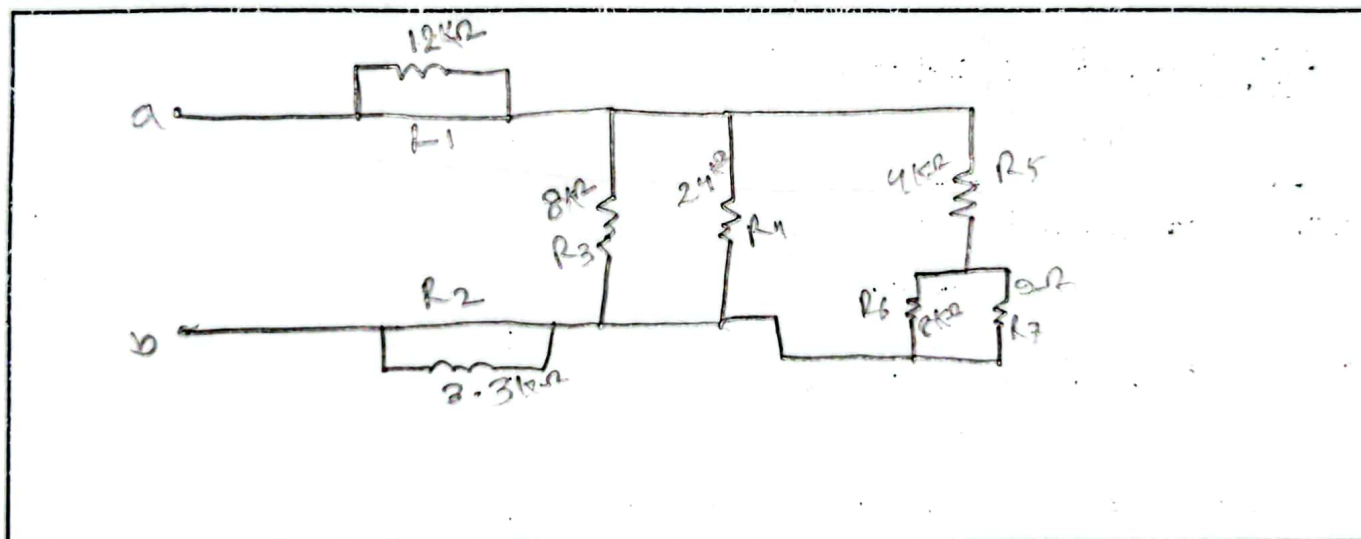(c) Based on the table in (b), draw a simplified version of the circuit using the labeled/identified nodes.



(d) Determine the equivalent resistance between terminals a and b from the reduced circuit drawn in (c).


$$R_{eq} = \left( \frac{1}{64} + \frac{1}{8} \right)^{-1}$$

$$= 6 \text{ k}\Omega$$



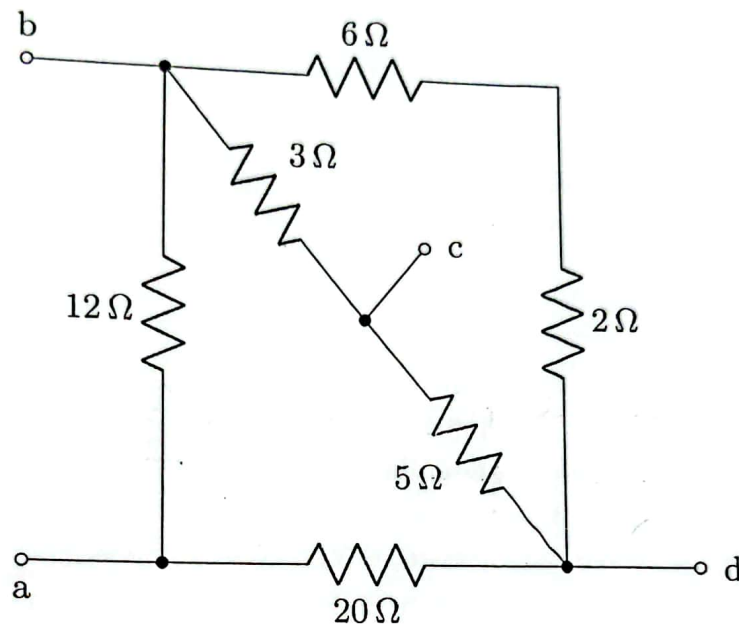5. For the following circuit, determine  $R_{ab}$ ,  $R_{ac}$ ,  $R_{ad}$ ,  $R_{bd}$  and  $R_{cd}$ . Use logical operators to indicate the series-parallel combinations. For example, the following equation means, two  $10\ \Omega$  resistors are in parallel, their combination is in series with a  $5\ \Omega$  resistor, and the total is again parallel with a  $20\ \Omega$  resistor.

$$R_{xy} = \{(10 \parallel 10) + 5\} \parallel 20$$



$R_{ab} = \{(2+6) \parallel (5+3) + 20\} \parallel 12\ \Omega$ $=$	$R_{ac} = (12+3) \parallel (20+5)$ $=$
$R_{ad} = (5+3) \parallel (5+3) + 12 \parallel 20$ $=$	$R_{bd} = (12+20) \parallel 8 \parallel 8$ $=$
$R_{cd} = ((20+12) \parallel (6+2) + 3) \parallel 5$ $=$	

## Report

1. Fill up the theoretical parts of all the data tables.
2. Answer to the questions.
3. Discussion [your overall experience, accuracy of the measured data, difficulties experienced and your thoughts on those]. Add pages if necessary.