



Student ID:	21201031	Lab Section:	24
Name:	Maisha Fairouz	Lab Group:	06

**Experiment No. 2****Verification of KVL & KCL****Objective**


The aim of this experiment is to use multi-loops and various branch circuits to verify Kirchhoff's voltage law (KVL) and Kirchhoff's current law (KCL).

**Apparatus**

- Multimeter
- Resistors (1 k $\Omega$  x 2, 2.2 k $\Omega$ , 3.3 k $\Omega$ , 4.7 k $\Omega$ ).
- DC power supply
- Breadboard
- Jumper wires

**Part 1: KVL****Theory**

KVL stands for Kirchhoff's Voltage Law, which is a fundamental principle used in electrical engineering and physics. It states that the sum of all the voltages in a closed loop in a circuit is equal to zero (Alternatively, it can be said that around any closed circuit the algebraic sum of the voltage rises equals the algebraic sum of the voltage drops).

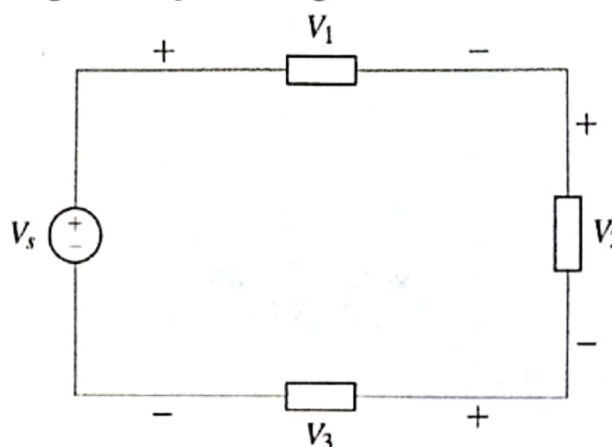

**Figure 1: Illustration of KVL**

To illustrate KVL, consider Fig. 1. The sign on each voltage is the polarity of the terminal encountered first as we travel around the loop. Let us start with the voltage source and go around the top, then voltages would be  $-V_s + V_1 + V_2 + V_3$ . Thus, KVL yields,

$$\sum \Delta V = -V_s + V_1 + V_2 + V_3 = 0$$


$$\Rightarrow V_s = V_1 + V_2 + V_3$$

Which can be interpreted as,

**Sum of voltage rises = Sum of voltage drops**

### Procedures

- Measure the resistances of the provided resistors and fill up the data table.
- Construct the following circuit on a breadboard. Try to use minimum number of jumper wires:

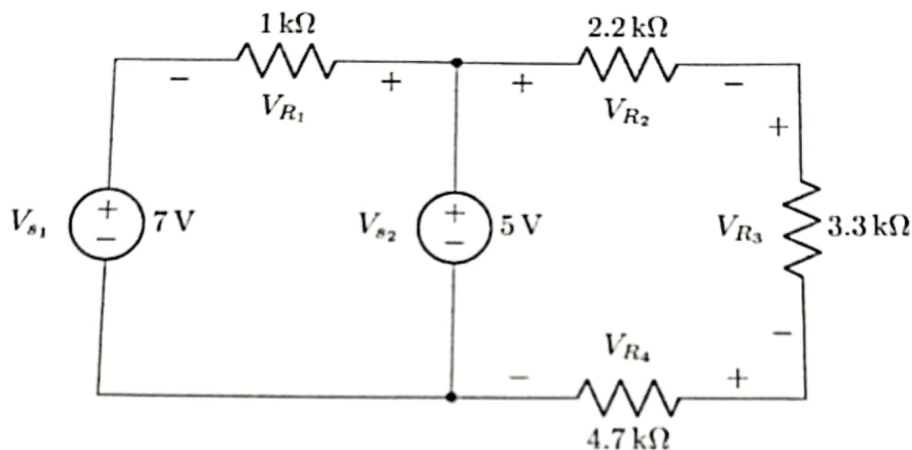

**Circuit 1**

- Measure the voltage across each resistor ( $V_{R_1}$ ,  $V_{R_2}$ ,  $V_{R_3}$ ,  $V_{R_4}$ ) as shown in the figure above. Fill up the data tables.
- Verify KVL as  $\sum \Delta V = 0$  for each loop (take the polarity of the resistors clockwise).

For the left sided loop,  $\sum \Delta V = -V_{s_1} - V_{R_1} + V_{s_2}$

For the right sided loop,  $\sum \Delta V = -V_{s_2} + V_{R_2} + V_{R_3} + V_{R_4}$

- Calculate the theoretical values of  $V_{R_1}$ ,  $V_{R_2}$ ,  $V_{R_3}$ ,  $V_{R_4}$  and note them down in the 'Theoretical Observation' row in Table 2 & 3. For  $V_{R_2}$ ,  $V_{R_3}$ ,  $V_{R_4}$  use the *Voltage Divider Rule*. Relevant formulas are given below for your convenience:

$$V_{R_1} = V_{s_1} - V_{s_2}$$

$$V_{R_2} = \frac{R_2}{R_s} \times V_{s_2}$$

$$V_{R_3} = \frac{R_3}{R_s} \times V_{s_2}$$

$$V_{R_4} = \frac{R_4}{R_s} \times V_{s_2}$$

where,  $R_s = R_2 + R_3 + R_4$

### Data Tables

Signature of Lab Faculty:

Jishnu

Date:

12/6/23

**\*\* For all the data tables, take data up to three decimal places, round to two, then enter into the table.**

**Table 1: Resistance Data**

For all your future calculations, please use the observed values only (even for theoretical calculations).

Notation	Expected Resistance	Observed Resistance (k $\Omega$ )
$R_1$	1 k $\Omega$	1.001
$R_2$	2.2 k $\Omega$	2.166
$R_3$	3.3 k $\Omega$	3.228
$R_4$	4.7 k $\Omega$	4.56

**Table 2: Data for Loop 1 (Left sided loop)**

In the following table,  $V_{R1}$  is the voltage drop across resistor  $R_1$ . Similar syntax applies to remaining resistors. Also, calculate the percentage of error between experimental and theoretical values of  $\sum \Delta V$ .

Observation	$V_{s1}$ (V) (from dc power supply)	$V_{s1}$ (V) (using multimeter)	$V_{s2}$ (V) (from dc power supply)	$V_{s2}$ (V) (using multimeter)	$V_{R1}$ (V)	$\sum \Delta V =$ $-V_{s1} - V_{R1} + V_{s2}$ (V)
Experimental	7	7.02	5	5.06	-1.95	-0.04
Theoretical	7		5		1.96	0

$$\text{Absolute error} = | \text{Experimental value} - \text{Theoretical value} |$$

Here, Absolute error in  $\sum \Delta V$  calculation =

0.04

**Table 3: Data for Loop 2 (Right sided loop)**

In the following table,  $V_{R2}$  is the voltage drop across resistor  $R_2$ . Similar syntax applies to remaining resistors. Also, calculate the percentage of error between experimental and theoretical values of  $\sum \Delta V$ .

Observation	$V_{s2}$ (V) (from dc power supply)	$V_{s2}$ (V) (using multimeter)	$V_{R2}$ (V)	$V_{R3}$ (V)	$V_{R4}$ (V)	$\sum \Delta V =$ $-V_{s2} + V_{R2} + V_{R3} + V_{R4}$ (V)
Experimental	5	5.06	1.098	2.32	1.635	0.007
Theoretical	5		1.088	1.641	2.291	0

Here, Absolute error in  $\sum \Delta V$  calculation =

0.007

### Questions

1. Let us take a look at **Circuit 1** again. If we remove the 5V voltage source ( $V_{s2}$ ) from the middle, the remaining circuitry contains only one big loop (often referred to as the outer loop). Let us examine if KVL holds true for the outer loop too.

- (a) Do you think KVL will be applicable to the outer loop?

☒ Yes ☐ No

Justify your answer.

KVL (Kirchoff's voltage law) will be applicable to the outer loop because voltages can be measured in <sup>series</sup> ~~parallel~~ by using voltmeter.

- (b) Use the values of  $V_{R1}$ ,  $V_{R2}$ ,  $V_{R3}$ ,  $V_{R4}$ ,  $V_{s1}$  from Tables 2 & 3 to verify your answer from the above question.

$$\sum \Delta V = -V_{s1} - V_{R1} + V_{R2} + V_{R3} + V_{R4} =$$

-0.017

Did KVL hold true for the outer loop?


☒ Yes ☐ No

Here, Absolute error in  $\sum \Delta V$  calculation =

0.017



2. For the following circuit,

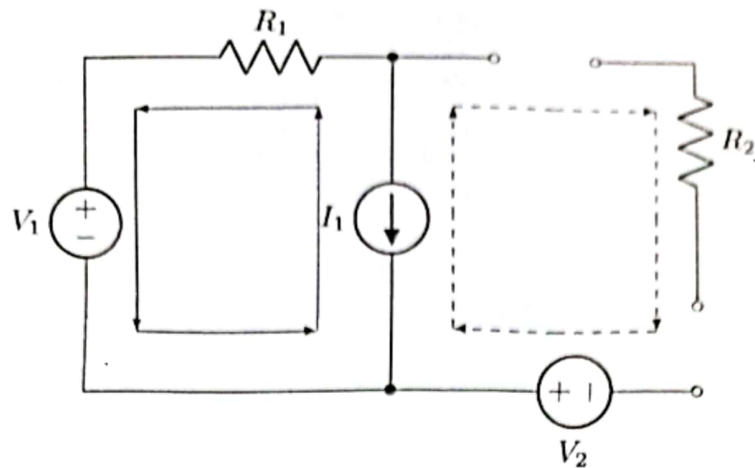

(a) Can we term the path represented by the solid line made up of  $V_1$ ,  $R_1$ , and  $I_1$  a loop?

☒ Yes      ☐ No


(b) Can we term the path represented by the dashed line made up of  $V_2$ ,  $R_2$ ,  $I_1$ , and open circuits a loop?

☐ Yes      ☒ No

(c) Based on your choices in (a) and (b), how would you define a loop?

A loop is a closed path going through the elements of a circuit. For drawing a loop, selecting any node as a starting point and it will travel every elements and comes back to starting point.

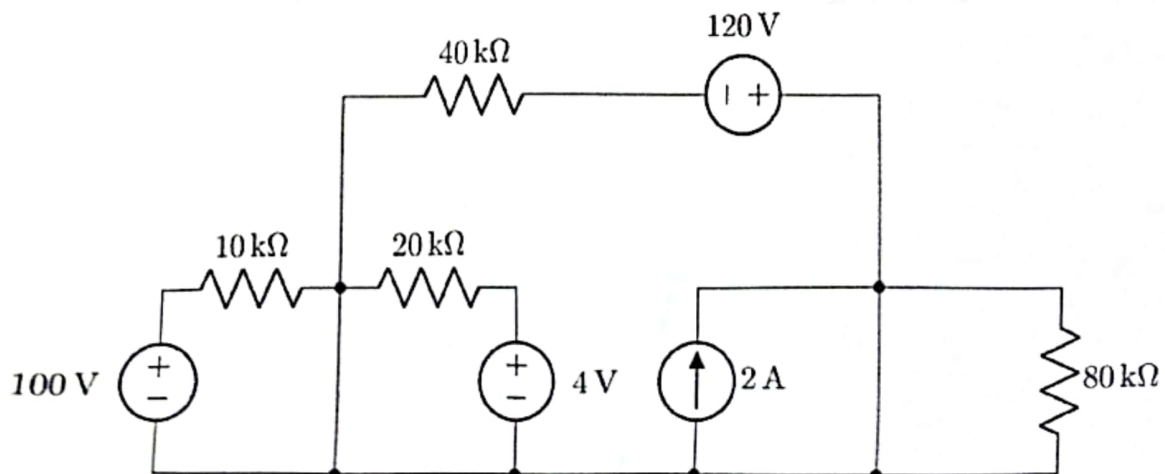
3. How many loops can you make for the following circuit? How many of them are 'Dependent' and how many are 'Independent'?



Number of independent loops = 5

Number of dependent loops = 1

4. For the following circuit,

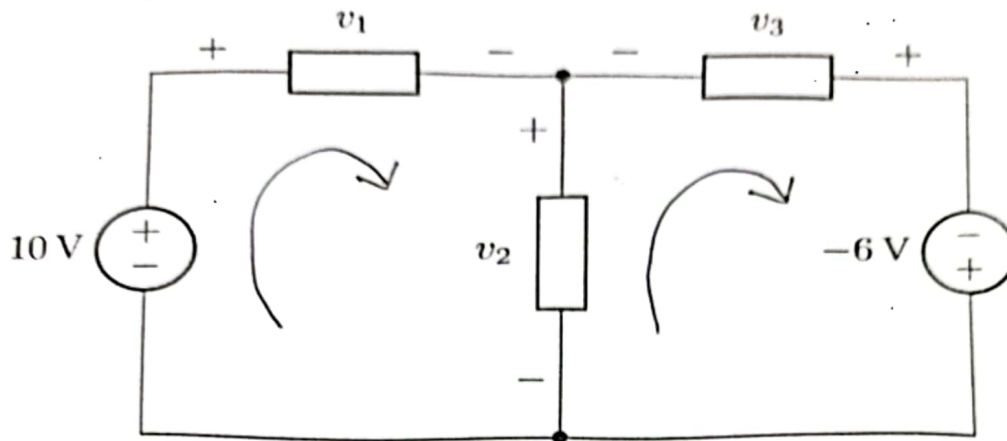

(a) How many loops may KVL be applied along? Mark the loops in the circuit diagram.

There are 2 loops.

(b) List all of the equations obtained by applying KVL along the number of loops mentioned in (a).

$$\sum V = 0$$

$$-10V + v_1 + v_2 = 0 \quad \text{--- (i)}$$

$$-v_2 - v_3 - (-6) = 0$$

$$-v_2 - v_3 + 6 = 0 \quad \text{--- (ii)}$$

(c) Can you observe any relationship among the equations? Is it possible to deduce any equation from the others? If so, show the deduction.

Yes.

Here,  $v_2$  is common in both the equations. No deduction is possible here.

(d) Now, have you been able to solve the simultaneous equations to get  $v_1$ ,  $v_2$ , and  $v_3$ ?

☐ Yes ☒ No

If yes, what are they? If not, why are the equations not solvable and what is your conclusion?

There were no sufficient data to solve these equations.

## Part 2: KCL

### Theory

KCL stands for Kirchhoff's Current Law, which is another fundamental principle used in electrical engineering and physics. It states that the total current entering a node in a circuit must equal the total current leaving the node. In other words, **KCL states that the algebraic sum of currents entering and exiting a node is equal to zero.** This law is also essential for analyzing circuits and predicting the behavior of electrical systems.

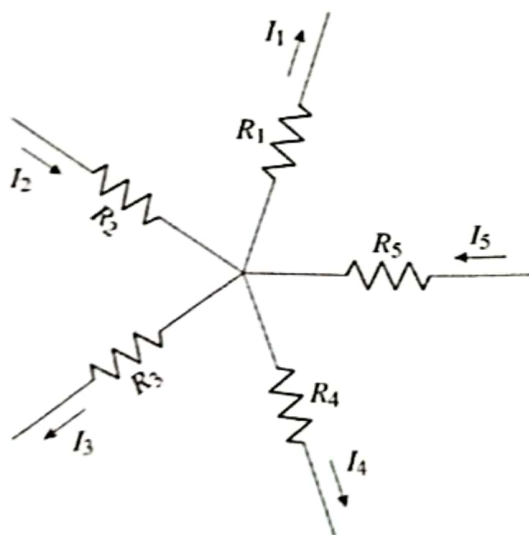


Figure 2: Illustration of KCL

To illustrate KCL, consider Fig. 2. Here, we can see 5 branches connected to 1 node. The exiting currents are  $I_1$ ,  $I_3$ ,  $I_4$  and the entering currents are  $I_2$ ,  $I_5$ . Applying KCL gives,

$$\sum i = I_1 + (-I_2) + I_3 + I_4 + (-I_5) = 0$$


$$\Rightarrow I_1 + I_3 + I_4 = I_2 + I_5$$

Which can be interpreted as,

**Sum of currents entering a node = Sum of currents leaving the node**

### Procedures

- Measure the resistances of the provided resistors and fill up the data table.
- Construct the following circuit on a breadboard. Try to use minimum number of jumper wires:

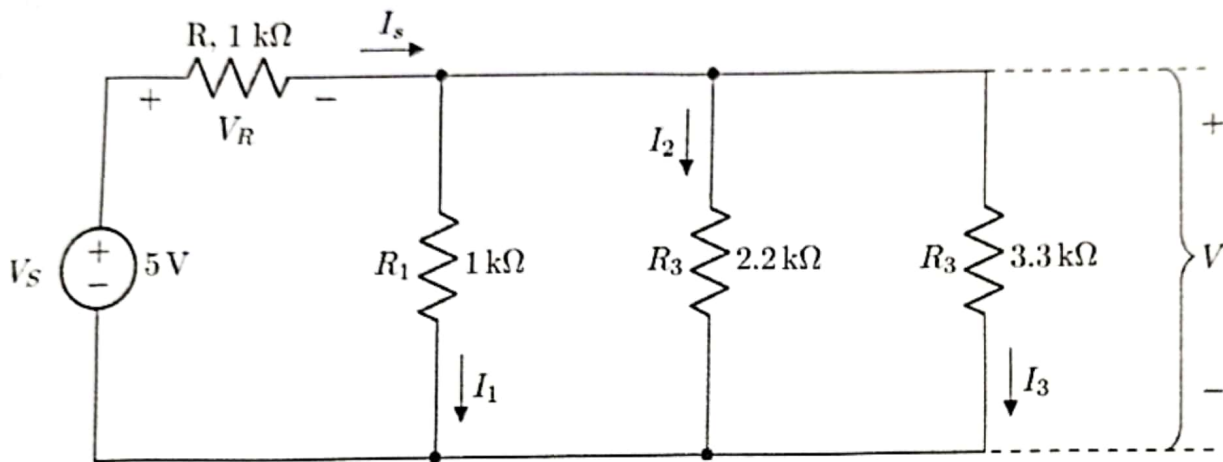

**Circuit 2**

- Measure the voltage and current across each resistor ( $V_R$ ,  $V$ ,  $I_s$ ,  $I_1$ ,  $I_2$ , &  $I_3$ ) as shown in the figure above. Use a Multimeter to measure the voltage, and use Ohm's law to calculate the current through each resistor. Fill up the data tables.
- Verify KCL as  $\sum i = 0$  for the node connecting  $R$  to  $R_1$ ,  $R_2$ , &  $R_3$  (Assume positive exiting currents).

For this node, 
$$\sum i = -I_s + I_1 + I_2 + I_3$$

- Calculate the theoretical values of  $I$ ,  $I_1$ ,  $I_2$ ,  $I_3$  and note them down in the 'Theoretical Observation' row in Table 5. For  $I_1$ ,  $I_2$ , &  $I_3$  use the *Current Divider Rule*. Relevant formulas are given below for your convenience:

$$I = \frac{V_s}{R + R_p}$$

$$I_1 = \frac{(R_1)^{-1}}{(R_p)^{-1}} \times I_s \quad I_2 = \frac{(R_2)^{-1}}{(R_p)^{-1}} \times I_s$$

$$I_3 = \frac{(R_3)^{-1}}{(R_p)^{-1}} \times I_s \quad \text{where } R_p = \left( (R_1)^{-1} + (R_2)^{-1} + (R_3)^{-1} \right)^{-1}$$



## Data Tables

Signature of Lab Faculty:

Date:

**\*\* For all the data tables, take data up to three decimal places, round to two, then enter into the table.**

**Table 4: Resistance Data**

For all your future calculations, please use the observed values only (even for theoretical calculations).

Notation	Expected Resistance	Observed Resistance (k $\Omega$ )
$R$	1 k $\Omega$	1.001
$R_1$	1 k $\Omega$	1.012
$R_2$	2.2 k $\Omega$	2.166
$R_3$	3.3 k $\Omega$	3.228

**Table 5: Data from Circuit 2**

In the following table,  $I_1$  is the current through resistor  $R_1$ . Similar syntax applies to remaining resistors. The voltage supplied to the complete circuit is denoted by  $V_s$  and the current being supplied to the whole network is denoted as  $I_s$ . Also, calculate the percentage of error between experimental and theoretical values of  $\sum i$ .

Observations	$V_s$ (V) (from dc power supply)	$V_s$ (V) (using multimeter)	$V_R$ (V)	$I_s = \frac{V_R}{R}$ (mA)	$V$ (V)	$I_1 = \frac{V}{R_1}$ (mA)	$I_2 = \frac{V}{R_2}$ (mA)	$I_3 = \frac{V}{R_3}$ (mA)	$\sum i = -I_s + I_1 + I_2 + I_3$ (mA)
Experimental	5	5.06	3.221	3.217	1.831	1.81	0.845	0.567	0.005
Theoretical	5		4.9	4.895	5	4.94	2.308	1.548	0

Here, Absolute error in  $\sum i$  calculation =


0.005

## Apparatus

- Multimeter
- Resistors ( 1k X2, 2.2k, 3.3k).
- DC power supply
- Breadboard
- Jumper wires

## Procedures

- Measure the resistances of the provided resistors and fill up the data table.
- Construct the following circuit on a breadboard. Try to use minimum number of jumper wires:

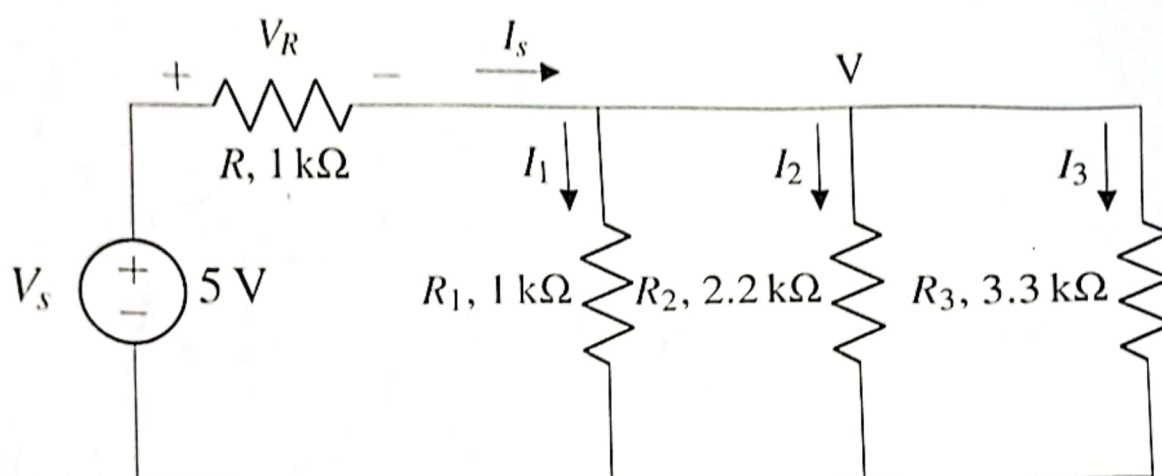

**Circuit 2**

- Measure the voltage and current across each resistor ( $V_R$ ,  $V$ ,  $I_s$ ,  $I_1$ ,  $I_2$ ,  $I_3$ ) as shown in the figure above. Use a Multimeter for measuring the voltage and use Ohm's law to calculate the current through each resistor. Fill up the data tables.
- Verify KCL as  $\sum i = 0$  for the node connecting  $R$  to  $R_1$ ,  $R_2$  &  $R_3$  (Assume positive exiting currents).

For this node, 
$$\sum i = -I_s + I_1 + I_2 + I_3$$

- Calculate the theoretical values of  $I$ ,  $I_1$ ,  $I_2$ ,  $I_3$  & note them down in the 'Theoretical Observation' row in Table 5. For  $I_1$ ,  $I_2$ ,  $I_3$  use the Current Divider Rule. Relevant formulas are given below for your convenience:

$$I = V_s / (R + R_p)$$

$$I_1 = \left( \frac{1/R_1}{1/R_p} \right) * I_s$$

$$I_2 = \left( \frac{1/R_2}{1/R_p} \right) * I_s$$

$$I_3 = \left( \frac{1/R_3}{1/R_p} \right) * I_s$$

Where,  $R_p = (1/R_1 + 1/R_2 + 1/R_3)^{-1}$

## Questions

5. Kirchhoff's current law (KCL) states that *the algebraic sum of branch currents flowing into and out of a node is equal to zero*. This is a consequence of another principle.


Which principle is it?

☐ Conservation of Energy    ☒ Conservation of Electric Charge    ☐ None of them

Why is your selection valid?

KCL is based on conservation of charge because at junction there is no accumulation of charge. The sum of total current at junction is zero.

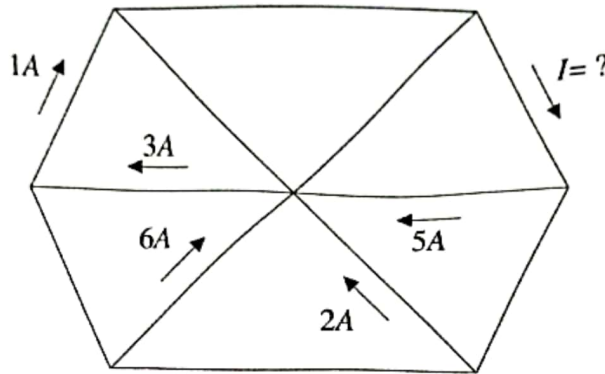6. Using KCL, determine the current  $I$  for the following circuit.




$$\sum I = 0$$

$$I_{\text{outgoing}} = I_{\text{incoming}}$$

$$= 1 + 6 + 2 + 5 - 3$$

$$= 11 \text{ A.}$$

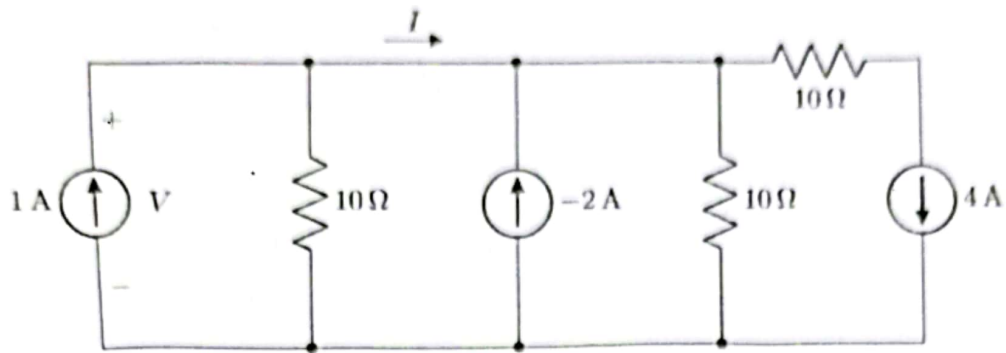7. For the following circuit, determine the current  $I$  using only KCL and Ohm's Law.




8.

(a) "KCL must always be applied at a node". The statement is-

☒ True      ☐ False

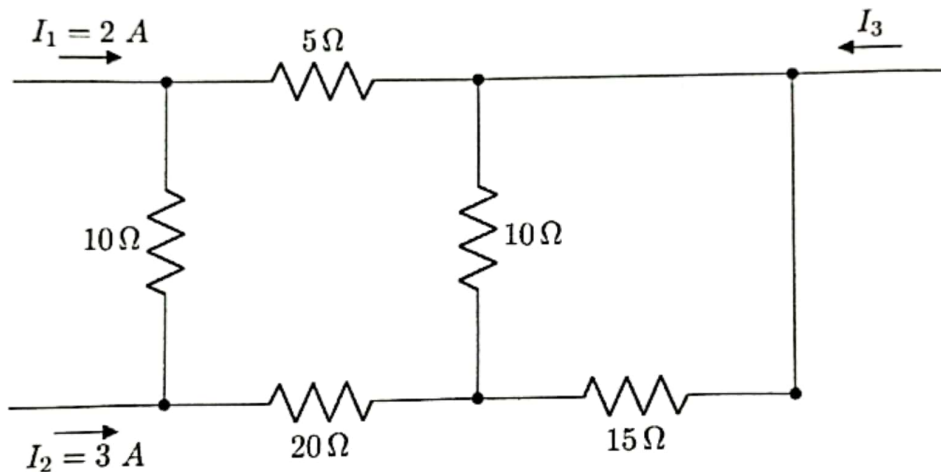(b) Using KCL only, determine the value of  $I_3$  if  $I_1 = 2\text{ A}$  and  $I_2 = 3\text{ A}$  in the circuit shown below.



$$\sum I = 0$$

$I_{\text{incoming}} = I_{\text{outgoing}}$

$$I_1 + I_3 = I_2$$

$$I_3 = I_2 - I_1$$

$$= 3 - 2$$

$$= 1\text{ A}$$

### **Report**

1. Fill up the theoretical parts of all the data tables.
  2. Answer to the questions.
  3. Comment on the obtained results and discrepancies. Start writing under the line.
-