

Student ID:	21201680	Lab Section:	15
Name:	Sadman Rahman Tasawar	Lab Group:	7

Experiment No. 3

Verification of Superposition Principle

Objective

The aim of this experiment is to verify experimentally the Superposition theorem which is an analytical technique of determining currents/voltages in a circuit with more than one emf source.

Theory

The Superposition Principle is a fundamental concept in electrical circuits that states that in any linear, active, bilateral network having more than one source, the response across any element is the sum of the responses obtained from each source considered separately and all other sources are replaced by their internal resistance. The superposition theorem is used to solve the network where two or more sources are present and connected. The current or voltage through any component in a circuit is the sum of the effects of each individual source acting alone. In other words, the principle states that **the total response of a circuit with multiple sources is the sum of the responses of the circuit to each individual source acting alone**. This principle is widely used in circuit analysis to simplify complex circuits and solve them with ease.

In a **linear circuit** containing multiple independent sources and linear elements (e.g., resistors, inductors, capacitors), the voltage across (or the current through) any element when all the sources are acting simultaneously may be obtained by adding algebraically all the individual voltages (or the currents) caused by each independent source acting alone, with all other sources deactivated.


An independent **voltage source** is deactivated (made zero) by **shorting** it and an independent **current source** is deactivated (made zero) by **open circuiting** it. However, if a dependent source is present, it must remain active during the superposition process.

Apparatus


- Multimeter
- Resistors (1k, 2.2k, 3.3k).
- DC power supply
- Breadboard
- Jumper wires

Procedures

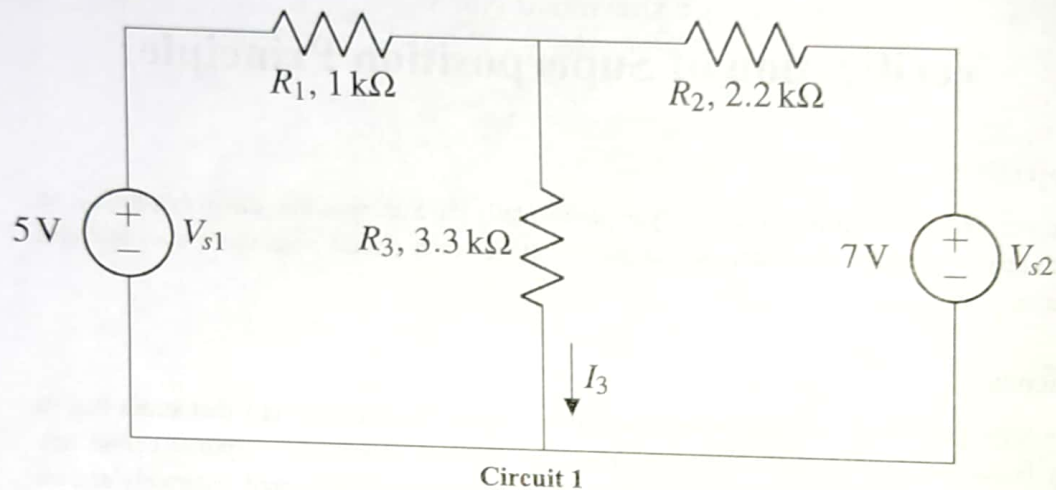
- Measure the resistances of the provided resistors and fill up the data table (Table 1).
- Construct the following circuit on a breadboard. Try to use minimum number of jumper wires:



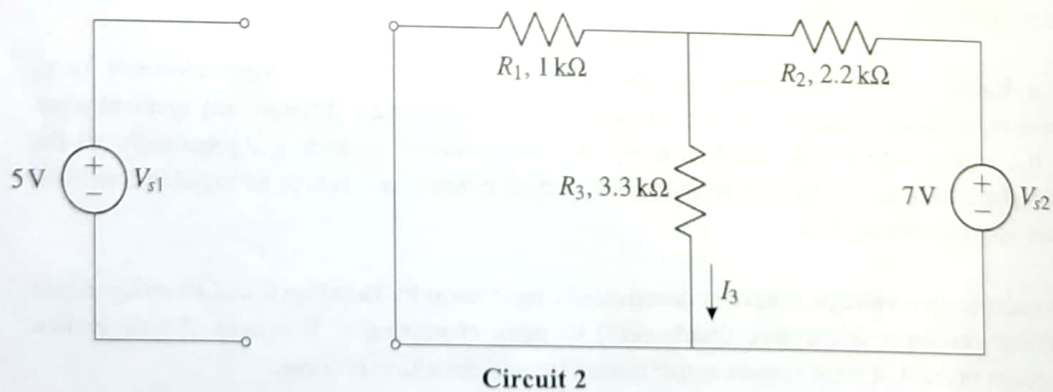- Measure the voltage across the resistors R_2 , R_3 and current through the resistor R_3 . Use a Multimeter for measuring the voltage and use Ohm's law to calculate the current (I_3) through R_3 . Fill up the data tables.
- Render V_{s1} inactive (keeping V_{s2} active) & Construct the following circuit.



- Measure the voltage across the resistors R_2 , R_3 and current through the resistor R_3 . Use a Multimeter for measuring the voltage and use Ohm's law to calculate the current (I_3') through R_3 . Fill up the data tables.
- Render V_{s2} inactive (keeping V_{s1} active) & Construct the following circuit.

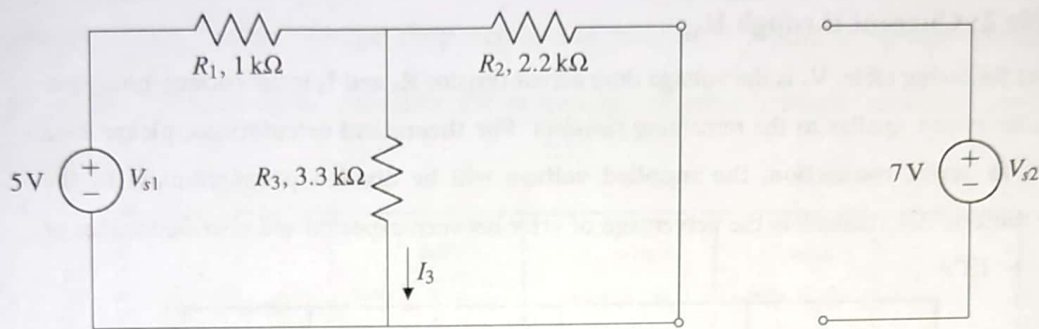

Circuit 3

- Measure the voltage across the resistors R_2 , R_3 and current through the resistor R_3 . Use a Multimeter for measuring the voltage and use Ohm's law to calculate the current (I_3) through R_3 . Fill up the data tables.
- Verify if $I_3 = I_3' + I_3''$ which would validate the superposition theorem for the current through R_3 .
- Verify if $V_2 = V_2' + V_2''$ which would validate the superposition theorem for the voltage across R_2 .

Data Tables

Signature of Lab Faculty:

[Handwritten Signature]

Date:

13/4/23

**** For all the data tables, take data up to three decimal places, round to two, then enter into the table.**

Table 1: Resistance Data

For all your future calculations, please use the observed values only (even for theoretical calculations).

Notation	Expected Resistance	Observed Resistance ($k\Omega$)
R_1	1 $k\Omega$	0.98
R_2	2.2 $k\Omega$	2.16
R_3	3.3 $k\Omega$	3.24

Table 2: Current through R_3 and voltage across R_2

In the following table, V_3 is the voltage drop across the resistor, R_3 and I_3 is the current through it. V_2 is the voltage drop across the resistor R_2 . Similar syntax applies to the remaining resistors. Also, calculate the percentage of error between expected and observed values of $I_3' + I_3''$.

Observation	I_3 with both V_1 and V_2 active (mA)	I_3' with only V_1 is active (mA)	I_3'' with only V_2 is active (mA)	$I_3' + I_3''$ (mA)
Experimental	1.441	0.878	0.558	1.43
Theoretical	1.434	0.877	0.557	1.434
Observation	V_{R_2} with both V_1 and V_2 active (V)	V_{R_2}' with only V_1 is active (V)	V_{R_2}'' with only V_2 is active (V)	$V_{R_2}' + V_{R_2}''$ (V)
Experimental	-2.33	2.842	-9.19	-2.34
Theoretical	-2.34	2.819	-9.18	-2.361

• **Percentage of error** = $\left| \frac{\text{Observed Value} - \text{Expected Value}}{\text{Expected Value}} \right| \times 100\%$

N.B: Here, the Expected values are I_3 , V_{R_2} and the Observed values are $I_3' + I_3''$ and $V_{R_2}' + V_{R_2}''$ respectively.

Hence, Percentage of error in $I_3' + I_3''$ calculation = 0.76 %

Hence, Percentage of error in $V_{R_2}' + V_{R_2}''$ calculation = 0.43 %

Questions

1. Calculate the **power associated** with R_2 using the experimentally measured values of currents or voltages when:

- Only V_1 source is active.
- Only V_2 source is active.
- Both V_1 and V_2 sources are active.

Fill out the Table given below and verify, whether the superposition theorem is verified or not in this case. If not, comment on the reasons. **You don't need to take any new readings for this task.** Use previous data from Table 2 to calculate the power. Remember, power consumed by a resistor, $P = VI = I^2R = \frac{V^2}{R}$

Observation	P_{R_2} when both V_1 and V_2 are active $P_{R_2} = \frac{V_{R_2}^2}{R_2}$ (W)	P_{R_2}' when only V_1 is active $P_{R_2}' = \frac{V_{R_2}^{'2}}{R_2}$ (W)	P_{R_2}'' when only V_2 is active $P_{R_2}'' = \frac{V_{R_2}^{''2}}{R_2}$ (W)	$P_{R_2}' + P_{R_2}''$ (W)
Experimental	2.513	3.739	12.476	16.209
Theoretical	2.489	3.664	12.196	15.863

Is the Superposition Principle applicable in the case of Power?

☐ Yes

☒ No


How would you relate your findings from this to the concept of linearity? Why does/doesn't it work when it comes to Power?

From Ohm's law we know, $V=IR \therefore V \propto I$, so it is linear. When it comes to power it may work. For example, in a simple circuit with a fixed resistance if the voltage is doubled the current flow will be doubled. Linearity may not work in some complex scenarios. It may not work due to factors like semiconductor properties, switching mechanisms or thermal effect.

2. Why was a short circuit wire required to be connected between the corresponding terminals while turning off a voltage source? Why wasn't simply turning off the power switch enough to deactivate the source?


When a voltage source is connected to a circuit, it stores electrical energy that remains in the system even after the power source is disconnected. That's why short circuit wire is required.

3. For the circuit shown below,

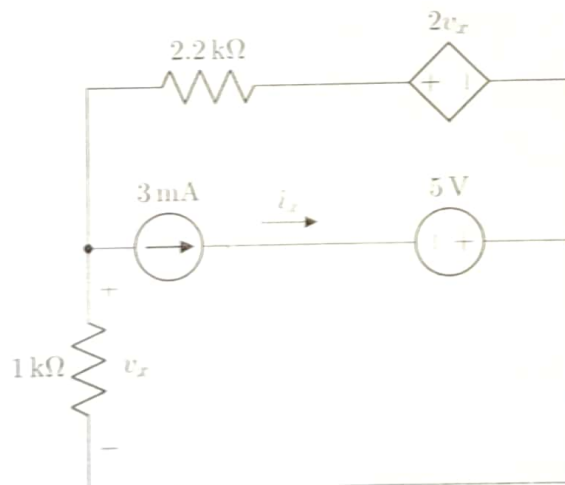

- (a) Show using the Superposition Principle that the 5 V voltage source has no effect on the current i_x .

Using the superposition principle for 5V

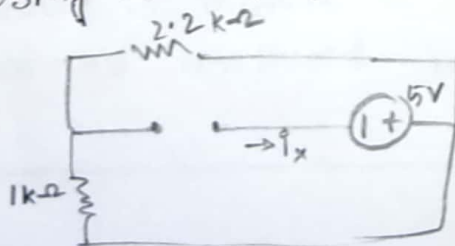

as it is a open circuit, there is no current flow through i_x , so, $i_x = 0 = I_1$

If 3mA current source is the only source only I_2 works.

According to superposition principle:

$$I_1 + I_2 = I_x$$

$$0 + I_2 = I_x$$

$$I_2 = I_x$$

\therefore 5V has no effect on i_x

(b) Why the 5 V voltage source does not contribute to the current i_x ?

As 3mA current taken out the circuit becomes open and no current can flow through the wire. So i_x becomes 0. That's why 5V voltage source does not contribute to the current i_x .

(c) Can you draw any conclusions about the resistances of an ideal voltage and current source from this? If so, what are they?

As the resistance of an ideal ~~circuit~~ voltage source is zero, that's why shared current can flow easily. The resistance of ideal current source is infinite as when the circuit is open no current can pass.

Report

1. Fill up the theoretical parts of all the data tables.
2. Answer to the questions.
3. Comment on the obtained results and discrepancies. Use the next page.